
LAB - 05


陳培殷老師 國立成功大學 資訊工程系

 

Introduction




■ 下載網址 - https://reurl.cc/eOQK7Q

 


■ 解壓縮後打開 setup.bat




Next

 

■ 勾選選項

 

 - 完成後勾選 Launch USB Blaster II driver installation



■ 跳出裝置驅動程式安裝精靈後一直按下一步




■ 出現 "可以使用"就完成安裝了




Quartus II Tutorial (1/19)

 - Getting Started
 - Start the Quartus II software




Quartus II Tutorial (2/19)

 - Create a New Project
 - Open New Project Wizard (File → New Project Wizard...)




Quartus II Tutorial (3/19)

 Specify the working directory and the name of the project



Quartus II Tutorial (4/19)

 - Select "Empty project". Then, click "Next".
- Select design files. Or click "Next" to skip this step.




Quartus II Tutorial (5/19)

Specify device settings - (DE10-Lite Device family are used). Click "Next."


MAX 10(DA/DF/DC/SA/SC)

10M50DAF484C7G

 


Quartus II Tutorial (6/19)

 
Specify EDA Tool – (Modelsim-Altera is selected for simulation). Click "Finish."



Quartus II Tutorial (7/19)

 - Edit a new file by opening a Verilog HDL file
 - □ (File → New → Verilog HDL File → OK)



 


Quartus II Tutorial (8/19)

Write Verilog code

Top module name 一定要跟 Project name 相同!!


輸入 (input)		輸出 (output)	
被加數 (a)	加數 (b)	和 (sum)	進位 (carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

```
module test (
  input a,
  input b,
  output sum,
  output carry
);
/* Write your code here. */
endmodule
```


Quartus II Tutorial (9/19)

 - **Compiling the Designed Circuit (synthesis 合成)**
 - □ (Processing → Start Compilation)



Quartus II Tutorial (10/19)


Successful compilation

 


Quartus II Tutorial (11/19)

Edit a new file by opening a Verilog HDL file

 
□ (File → New → University Program VWF → OK)



 


Quartus II Simulation (12/19)

 - Simulating the Designed Circuit
 - Use node finder to find all the I/O pins (Edit → Insert → Insert Node or Bus...)




Quartus II Simulation (13/19)

 - Simulating the Designed Circuit
 - Selecting nodes to insert into the Waveform Editor




Quartus II Simulation (14/19)

 
- Simulating the Designed Circuit
 - Selecting nodes to insert into the Waveform Editor



Quartus II Simulation (15/19)

 
- Simulating the Designed Circuit
 - Select and edit waveform



 


Quartus II Simulation (16/19)

 - Simulating the Designed Circuit
 - Setting of test values




Quartus II Simulation (17/19)

 - Simulating the Designed Circuit
 - Run Functional Simulation




Quartus II Simulation (18/19)

 
- Simulating the Designed Circuit
 - Save .vwf



Quartus II Simulation (19/19)


The result of functional simulation

 

 


Quartus II Simulation Notice

- 如果 simulation 時出現 error ,修改 ModelSim-Altera 路徑
 - □ 個人電腦: (Tools → Options → EDA Tool Options → ModelSim-Altera → C:\intelFPGA_lite\18.1\modelsim_ase\win32aloem)
 - □ 實驗室電腦:(Tools → Options → EDA Tool Options → ModelSim-Altera → C:\intelFPGA\16.1\modelsim_ase\win32aloem)

 


Lab I - Half Adder

a\b	0	1
0	0	1
1	1	0

 

a\b	0	1	
0	0	0	
1	0	1	
c_out=ab			

 

Lab I - Half Adder

(a) Using Verilog to implement a 1-bit Half Adder

Please implement with 3 methods

- 1) Structural description
- 2) Data flow description
- 3) Behavioral description

(b) Simulation with waveform

Lab I - Hint


Structural Description

Verilog allows three kinds of descriptions for circuits:

(1) Structural description (2) Data flow description (3) Behavioral description

Structural description:

- module OR_AND_STRUCTURAL(IN,OUT);
- input [3:0] IN;
- output
 OUT;
- wire [1:0] TEMP;
- or u1(TEMP[0], IN[0], IN[1]);
- or u2(TEMP[1], IN[2], IN[3]);
- and (OUT, TEMP[0], TEMP[1]);
- 8. endmodule

 

Lab I - Hint

Data Flow Description

Data flow description

Lab I - Hint


Behavioral (RTL) Description

Behavioral description


```
    module OR_AND_BEHAVIORAL(IN, OUT);
```

```
input [3:0] IN;output OUT;
```

- 4. reg OUT;
- 5. always @(IN)
- 6. begin
- 7. OUT = (IN[0] | IN[1]) & (IN[2] | IN[3]);
- 8. end
- 9. endmodule

 

Lab I - Simulation with waveform

 



a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Lab II - Full Adder (1/2)

ab\c_in	0	1
00	0	1
01	1	0
11	0	1
10	1	0

ab\c_in	0	1
00	0	0
01	0	1
11	1	1
10	0	1

sum

$$=(ab+ab)c_in+(ab+ab)c_in$$

$$=(a \oplus b)c_{in}+(a \oplus b)c_{in}$$


$$= (a \oplus b) \oplus c_{in}$$

$$=ab+(ab+ab)c_in$$

$$=ab+(a\oplus b)c_in$$

Lab II - Full Adder (2/2)

You can implement a full adder with (2 half adder and 1 or gate).

 

Lab II - Full Adder


(a) Using Verilog to implement a 1-bit Full Adder

Please implement with 3 methods

- 1) Structural description(with 2 half adder + 1 or gate)
- 2) Data flow description
- 3) Behavioral description

(b) Simulation with waveform

Lab II - Simulation with waveform

 

Z	y	X	S	С
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Notice

- 請勿在桌面建立 Project 及請勿命名中文資料夾
- Device family 請確認與 FPGA Chip 符合 (10M50DAF484C7G)
- Top module name & Project name 需要一致
- 確認 module ... endmodule 為 keyword 變成藍色字體